

## Lab2\_110550085

(1)

Half Subtractor

Truth Table:


a	b	diff	bout
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Boolean Expression:


$$\text{diff} = a \oplus b$$

$$\text{bout} = a'b$$

Logic Diagram:

 

The simulation:

 


We can know this result is correct by observing the truth table.

The propagation delay for bout is 2 time units, and for diff is 4 time units.


(2)

Full subtractor

Logic Diagram:

 

The simulation:

 

We can know this result is correct by observing the truth table.

The truth table:


Inputs			Outputs	
A	B	Borrow <sub>in</sub>	Diff	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Then, the propagation delay for diff is **8** time units, and so is bout.


In the simulation picture, we can see diff and bout have same propagation delay.

(3)


Logic Diagram:

 

The simulation:

 



 

We could know the three results are all correct by simply calculating it.

The propagation delay time for gatelevel modeling is **12** time units, which equals to

4(xnor for Pi)+2("or" to create terms of the SoP form)

+2("and" to sum all the terms)+4(xnor for Di, i=1, 2, or 3).

This can be observed clearly through the simulation wave.

(5)

Excess-3-to-binary-converter

The Karnaugh map for B[3], B[2], B[1], B[0], and v are:

AB \ CD	00	01	11	10
00	X	X	0	X
01	0	0	0	0
11	1	X	X	X
10	0	0	1	0

B[3]

AB \ CD	00	01	11	10
00	X	X	0	X
01	0	0	1	0
11	0	X	X	X
10	1	1	0	1

B[2]

AB		00	01	11	10
CD	00	X	X	0	X
	01	0	1	0	1
	11	0	X	X	X
	10	0	1	0	1

B[1]

AB		00	01	11	10
CD	00	X	X	0	X
	01	1	0	0	1
	11	1	X	X	X
	10	1	0	0	1

B[0]

AB		00	01	11	10
CD	00	0	0	1	0
	01	1	1	1	1
	11	1	0	0	0
	10	1	1	1	1

v

Where  $C=E[3]$ ,  $D=E[2]$ ,  $A=E[1]$ ,  $B=E[0]$ .

Thus, we could know the Boolean functions are:

$$B[3]=E[3]E[2]+E[3]E[1]E[0],$$


$$B[2]=E[2]'E[0]'+E[3]E[1]'E[0]+E[2]E[1]E[0],$$

$$B[1]=E[1]'E[0]+E[1]E[0]'=E[1]\oplus E[0],$$

$$B[0]=E[0]',$$


$$\begin{aligned} v &= E[3]'E[2]+E[3]E[2]'+E[3]E[1]'E[0]'+E[3]'E[1]E[0] \\ &= E[3]\oplus E[2]+E[3]E[1]'E[0]'+E[3]'E[1]E[0]. \end{aligned}$$

 Then we could draw the logic diagram for this converter:




The simulations are:


Gatelevel modeling:

 

Dataflow modeling:

 

Behavioral modeling:

 

The three results are all correct, since when  $v=1$ , all B's equal to  $E-3$ .

(6)

我覺得這次的 Lab 很有趣，讓我回想起了小時候在玩 Minecraft 時接電路的心情，從完成一個小電路(Half Subtractor)到接出相對大的機器(Ripple Borrow Subtractor)，令人相當有成就感。

這次的 Lab 中我也遭遇了不少挑戰，其一是會忘記上次 Lab 學過的東西，比如說一個 testbench 測 4 組測資時要把輸出改成不同代號，這樣他們的結果才不會互相影響，這點就困擾了我一段時間，後來討論時發現不是只有我有遇到這個問題。

另外，always 裡面的語法也困擾了我一段時間，最後寫出來的東西雖然是對的，但卻感覺難以實際應用，電機同學也說我把它當 Python 在寫，但我實在想不出，也討論不出更好的解法，只好這樣了。

另外，延遲的判定一直是我不拿手的地方，常常一個圖要看好幾次才能算對，這些都是我未來仍然值得精進的地方。